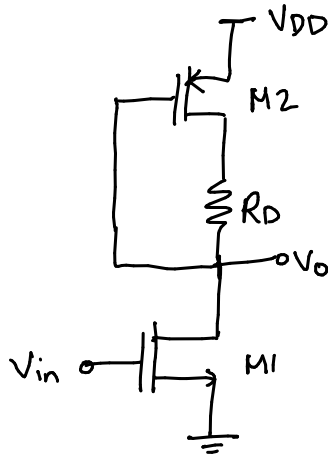


Tutorial 3 solutions : ELL304

Q Find the small signal gain A_v , assuming that both M1 & M2 are in saturation.



$$r_{o1} = r_{o2} = 1\text{M}\Omega, R_D = 10\text{K}\Omega$$


$$\left(\frac{W}{L}\right)_1 = 10, \left(\frac{W}{L}\right)_2 = 1$$

$$\text{Assume } \mu_n C_{ox} = \mu_p C_{ox} = 100 \mu\text{A}/\text{V}^2$$

$$V_{DSAT,1} = V_{DSAT,2} = 0.5\text{V}$$

The overall $G_m \approx -g_{m1}$ [$r_{o1}, R_D, g_{m2}, r_{o2}$ all vanish for I_{sc}]

For $R_{out} \rightarrow$

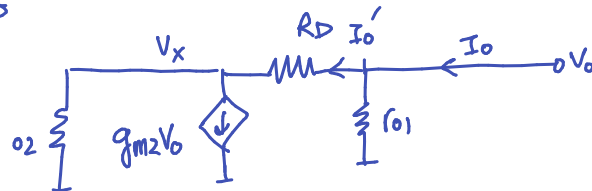

$$\frac{V_x}{r_{O2}} + g_{m2}V_o = I_o'$$

$$V_o - V_x = I_o' R_D$$

$$V_x = V_o - I_o' R_D$$

$$\frac{V_o - I_o' R_D}{r_{O2}} + g_{m2}V_o = I_o'$$

$$V_o \left(\frac{1}{r_{O2}} + g_{m2} \right) = I_o' \left(\frac{R_D}{r_{O2}} + 1 \right)$$

$$R_{out} = r_{O1} \parallel \frac{R_D/r_{O2} + 1}{1/r_{O2} + g_{m2}}$$


$$= r_{O1} \parallel \frac{R_D + r_{O2}}{1 + g_{m2}r_{O2}}$$

$$\text{small-signal gain} = \frac{V_{out}}{V_{in}} = G_m R_{out} = -g_{m1} \left(r_{O1} \parallel \frac{R_D + r_{O2}}{1 + g_{m2}r_{O2}} \right)$$


$$\approx -g_{m1} (r_{O1} \parallel 1/g_{m2})$$

$$\approx -g_{m1}/g_{m2}$$

Q2

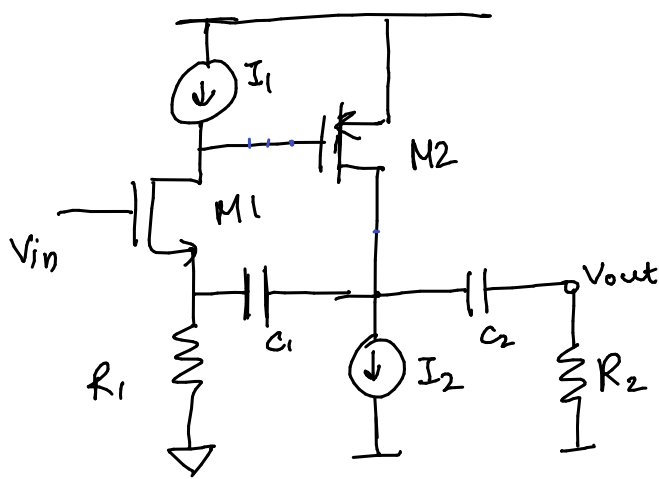

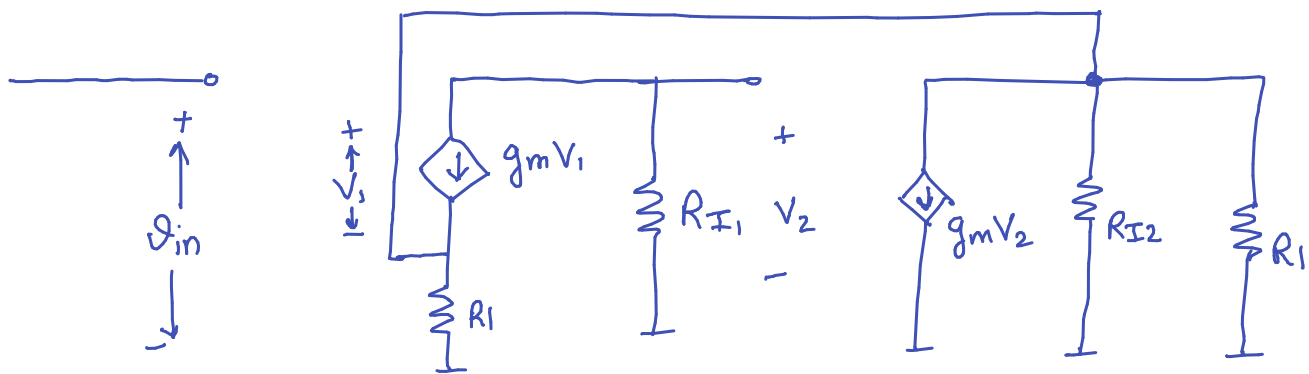Assume $M1$ & $M2$ are in satⁿ.
 I_1 and I_2 are non ideal current sources with shunt resistance of $10\text{ k}\Omega$
 C_1 & C_2 are large. Find the small signal DC gain. $\left(\frac{V_{out}}{V_{in}}\right)$.



$$V_1 = V_{in} - V_{out}$$

$$V_2 = - (g_{m1} V_1) R_{I1}$$

$$\Rightarrow g_{m1} V_1 = \frac{V_{out}}{R_1 \parallel R_2 \parallel R_{I2}} + g_{m2} V_2$$

$$g_{m1} (V_{in} - V_{out}) = \frac{V_{out}}{R'} - g_{m2} (g_{m1} (V_{in} - V_{out}) R_{I1})$$

$$[R' = R_1 \parallel R_2 \parallel R_{I2}]$$

$$V_{in} (g_m + g_m^2 R_{I1}) = V_{out} \left(\frac{1}{R'} + g_m + g_m^2 R_{I1} \right)$$

$$\frac{V_{out}}{V_{in}} = \frac{g_m (1 + g_m R_{I1})}{\frac{1}{R'} + g_m (1 + g_m R_{I1})}$$


- 03 In the circuit shown below, assume M_1 is biased in the saturation region using V_B and some external biasing. The overdrive voltage for M_1 is $0.2V$. Calculate the incremental input impedance (in Ω) for $R_1 = []$ and $R_2 = 10K\Omega$.

Other parameters:

$$V_{DD} = 3.3V$$

$$\mu_n C_{ox} = 300 \mu A/V^2$$

$$\left(\frac{W}{L}\right)_1 = 2.$$

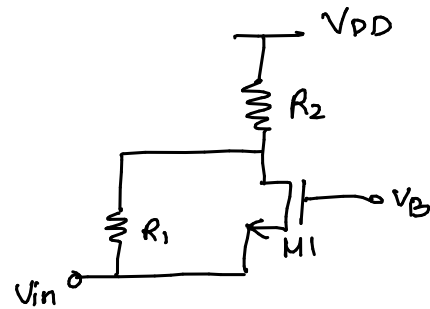


soln

Assume $R_1 = a$

$$a = 1000 * \pi \text{ where } 0.12 < \pi < 0.3 \text{ M}\Omega$$

$$g_{m1} = \mu_n C_{ox} \left(\frac{W}{L}\right)_1 V_{ov1} = 120 \mu S$$

For small signal R_{in}

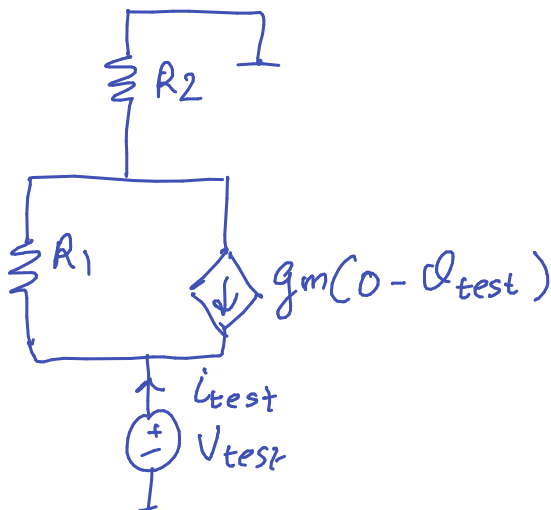

$$i_{test} = g_m v_{test} + \frac{v_{test} - R_2 i_{test}}{R_1}$$

$$\Rightarrow i_{test} \left(1 + \frac{R_2}{R_1}\right) = \left(g_m + \frac{1}{R_1}\right) v_{test}$$

$$\Rightarrow R_{in} = \frac{R_1 + R_2}{1 + g_m R_1}$$


$$= \frac{1000 * (\pi + 0.01)}{1 + (120 \mu S)(\pi)}$$

- 04 In the circuit shown below, $I_{BIAS} = 200 \mu A$. On injecting an incremental current i_s , an incremental voltage v_{out} is obtained across R_L . Consider R_L and R_G to be $[[R_L]] K\Omega$, and $[[R_G]] K\Omega$, find the ratio $\left| \frac{v_{out}}{i_s} \right|$ in $K\Omega$.

$$V_{DD} = 6V$$


$$V_{TN} = 1V$$

$$(W/L)_1 = 1$$

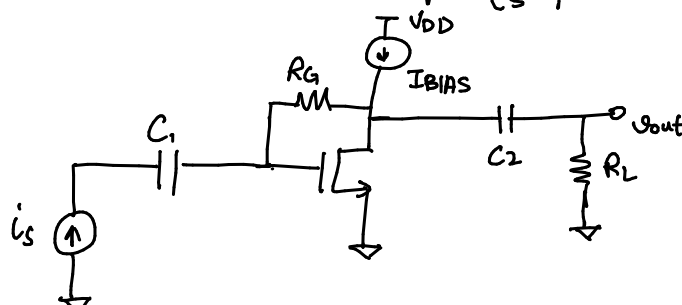

Assume C_1 & C_2 are very large and $\lambda = 0$.

Soln

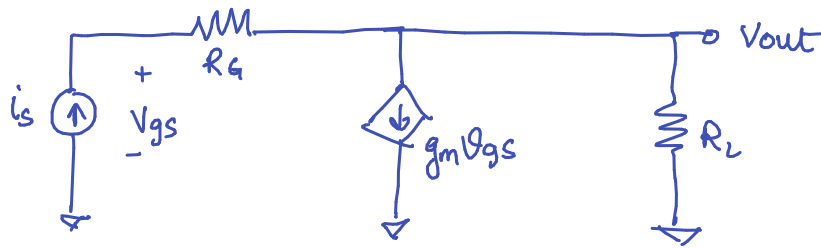

$$v_g = v_{out} + i_s R_G$$

$$g_m v_{gs} = g_m (v_{out} + i_s R_G)$$


$$i_s = g_m (v_{out} + i_s R_G) + \frac{v_{out}}{R_L}$$

$$v_{out} \left(g_m + \frac{1}{R_L} \right) = i_s (1 - g_m R_G) / (1 + g_m R_L)$$

$$\left| \frac{v_{out}}{i_s} \right| = \left| \frac{R_L (1 - g_m R_G)}{1 + g_m R_L} \right|$$

$$g_m = \sqrt{2 I_{BIAS} \mu_n C_{ox} \left(\frac{W}{L} \right)}$$

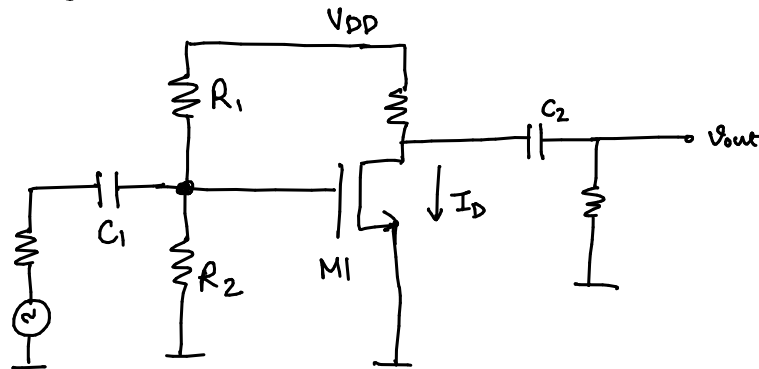Q In the circuit shown below, $V_{DD} = 5V$, $R_1 = 6.3M\Omega$, $R_2 = 2.7M\Omega$, $R_L = R_D$. Parameters of M_1 are $\mu_n C_{ox} = 200 \mu A/V^2$, $\left(\frac{W}{L} \right) = 6$ and $V_{TH} = 0.5V$. To prevent M_1 from going into triode, $V_{in} < V_1$. Find V_1 .



$$V_G = V_{DD} \left[\frac{R_2}{R_1 + R_2} \right] = 1.5V$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_T)^2 = 0.6mA$$

$$V_{DS} = V_{DD} - I_D R_D = 3.44V$$

$$g_m = \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_T) = 1.2mS$$

$$\text{Gain} = -g_m (R_D || R_L) = -1.56$$

To prevent M_1 from going into triode,

$$V_{DS, tot} > V_{GS, tot} - V_T$$


$$V_{DSO} - g_m (R_D || R_L) V_G > V_{GSO} + V_G - V_{TH}$$

$$\Rightarrow v_g < \frac{V_{DSD} - (V_{GSD} - V_{TH})}{1 + g_m(R_D \parallel R_L)} = 0.953$$

$$\therefore v_g = \frac{v_{in} (R_1 \parallel R_2)}{R_s + (R_1 \parallel R_2)} \approx v_{in}$$

$$\Rightarrow \boxed{v_{in} < 0.953}$$

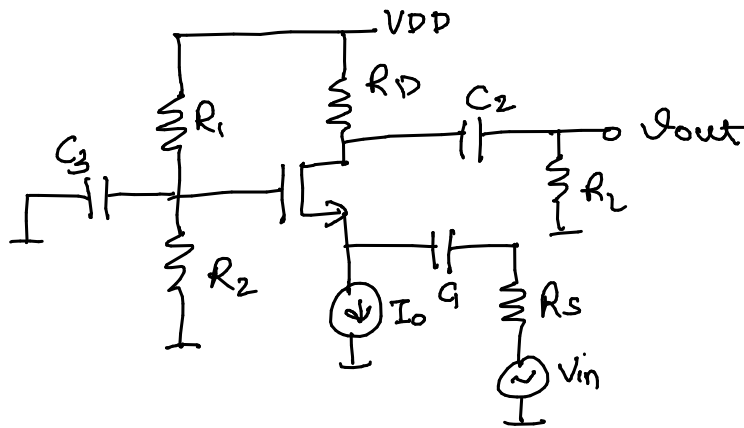Q $V_{DD} = 10V$, $R_1 = 4.2M\Omega$, $R_2 = 2.8M\Omega$, $R_s = 8.5K\Omega$, $R_L = R_D$. Source of M_1 is at $1.4V$. Drain and gate voltages are equal and $I_D = I_0$. $\mu_n C_{ox} = 100 \mu A/V^2$, $(\frac{W}{L})_1 = 1$ and $V_T = 1V$. Find small signal gain $\frac{v_{out}}{v_{in}}$.



$$V_G = \frac{R_2}{R_1 + R_2} V_{DD} = 4V$$

$$V_S = 1.4V \rightarrow V_{GS} = 2.6V$$

$$I_D = \frac{1}{2} \times (100 \times 10^{-6}) (2.6 - 1)^2 = 128 \mu A$$


$$g_m = \sqrt{2 I_D \mu_n C_{ox} \left(\frac{W}{L}\right)} = 160 \mu S$$

$$\frac{1}{g_m} = 6.25 K\Omega \quad (\text{impedance looking into source})$$

$$R_D = \left(\frac{V_{DD} - V_D}{I_D} \right) = \left(\frac{V_{DD} - V_G}{I_D} \right) = 46.875 K\Omega$$

$$\boxed{\frac{v_{out}}{v_{in}} = \left(\frac{Y_{gm}}{R_s + Y_{gm}} \right) \cdot g_m (R_D \parallel R_L) = 1.588}$$

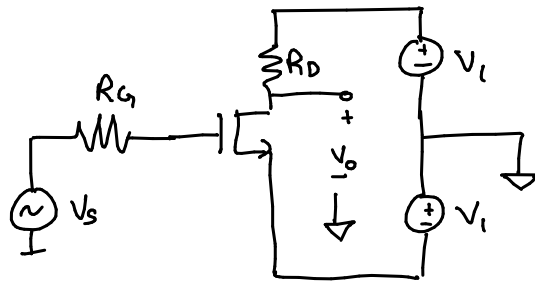Q The circuit shown below is a configuration where coupling capacitors can be eliminated. Find R_D (in $k\Omega$) such that voltage between drain and ground consists of only signal component. $V_1 = 2V$, $R_G = 55k\Omega$, $\mu_n C_{ox} = 50 \mu A/V^2$, $(\frac{W}{L}) = 9$, $V_T = 1V$.



Input DC voltage = $0V$
 $V_{GS} = 0 - (-2) = 2V$.

In order to eliminate requirement of coupling capacitors, DC potential at drain node should be $0V$.

$$V_{DS} = (0 - (-2)) = 2V$$

$$V_{DS} = V_{GS} \text{ (saturation)}$$


$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_T)^2 = 225 \mu A$$

$$\text{Voltage across } R_D = I_D R_D$$


$$(2 - 0) = (225 \mu A) R_D$$

$$\therefore R_D = 8.88 k\Omega$$

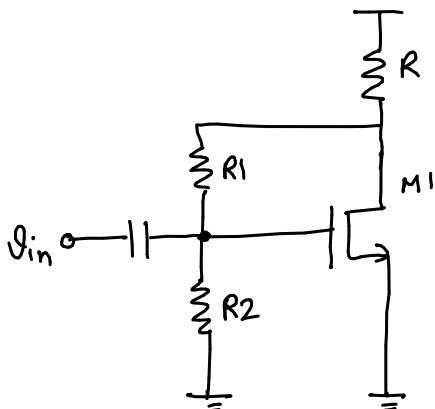Q For the given common-source amplifier, calculate the output impedance (in Ω). $R_1 = 168\Omega$, $R_2 = 200k\Omega$, $g_m = 5.01 mS$, $R = 115k\Omega$, $I_D = 50 \mu A$, $\lambda = 1 mV^{-1}$.



solⁿ

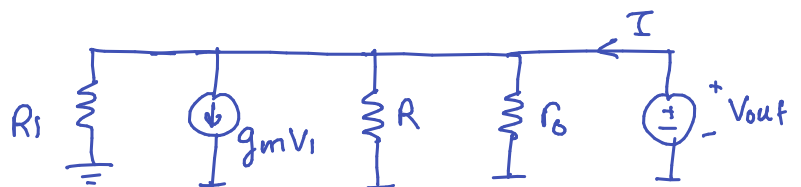

$$V_1 = 0 \Rightarrow g_m V_1 = 0$$

$$\frac{V_{out}}{I} = R_0 \parallel R \parallel R_1$$

$$= R_1 \quad (R_0 \gg R \gg R_1)$$

$$\approx 168\Omega$$