

Single Stage Amplifier Simulation  
Assignment 2  
ELL304

Yash Agarwal  
2021EE10638


November 15, 2023

**Contents**


<b>1</b>	<b>Question 1</b>	<b>2</b>
1.1	Part A . . . . .	2
1.2	Part B . . . . .	2
1.3	Conclusion . . . . .	3
<b>2</b>	<b>Question 2</b>	<b>3</b>
<b>3</b>	<b>Question 3</b>	<b>6</b>

# 1 Question 1


## 1.1 Part A

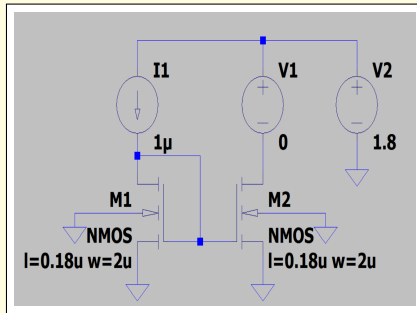


Circuit Schematics (L=0.18u)

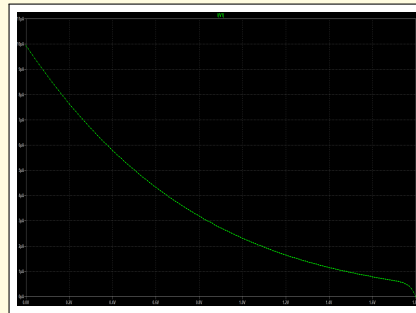

I vs V plot

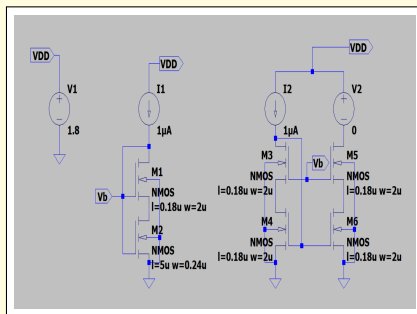


Circuit Schematics (L=0.18u)

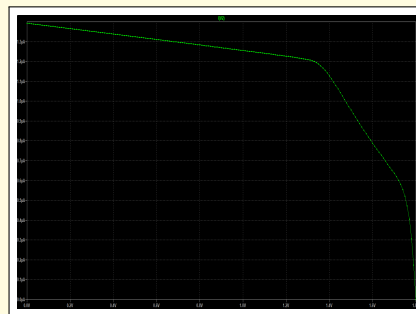

I vs V plot


## 1.2 Part B

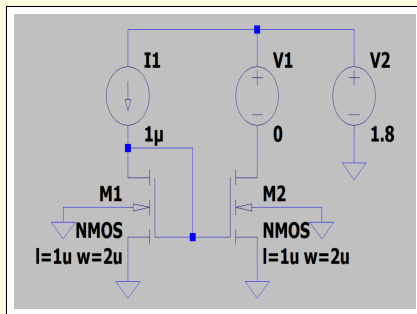


Circuit Schematics (L=1u)



I vs V plot

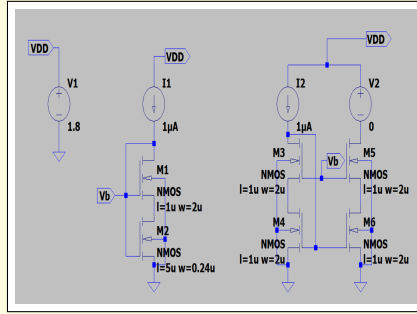

Circuit Schematics (L=1u)

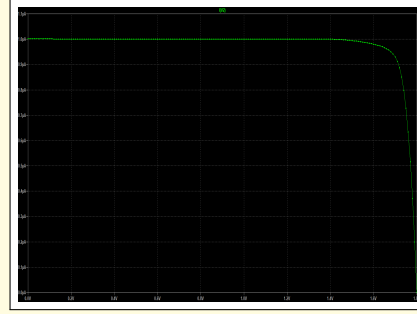


I vs V plot

### 1.3 Conclusion

- We see that the gain drops due to increase in L and process variations but the waveform of the variation of current remains the same.
- The extra current flows into parasitic capacitances and body of the MOSFETs, hence we can see a lot of non-ideality at edge of process limits (smaller transistors have more mismatches).
- As we increase L, we reduce the extra currents through the parasitic elements and observe more ideal mirroring action. We also have better output impedance.

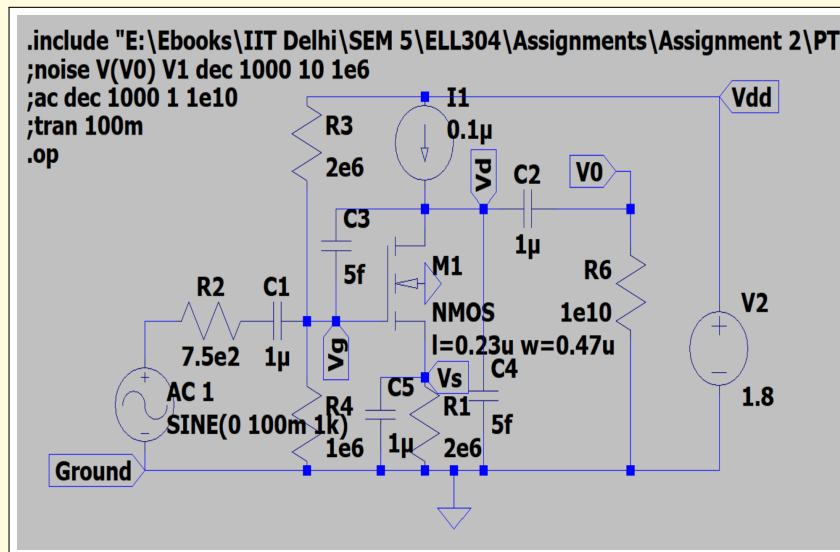
## 2 Question 2

- We need to design a CS Amplifier for a DC gain of 30dB and a Unity Gain Bandwidth of 50MHz while minimising power dissipation.
- The gain of a common source amplifier is approximately  $g_m \cdot r_0$
- A gain of 30dB is equivalent to a gain of 31.622 on the linear scale.
- $g_m \cdot r_0 = 2 / (V_{ov} \cdot \lambda)$ , thus we need to reduce the  $V_{ov}$  to get a better gain.
- We choose  $V_{gs} \approx V_T$  so that  $V_{ov} \approx 0$  and we get high gain.
- For low power dissipation, we reduce the MOS Current. Thus we take MOS current as  $0.1\mu$ . So that the power requirements are minimised.
- Choose  $R_L$  as high as possible so that it doesn't affect the gain of the amplifier. We choose it as  $1e10\Omega$ .
- We choose values of other resistors and capacitors accordingly to maintain gain and keep the device in saturation.



Circuit Schematics of the Amplifier

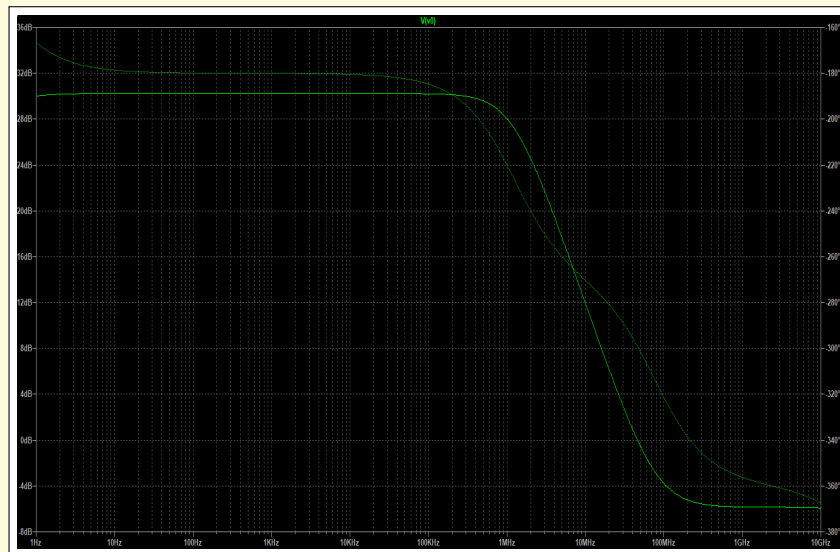- We adjust C3,C4 so that the UGB is as expected.
- The Device is in Saturation.
- We apply an AC signal of amplitude 1 and plot the AC Characteristics of the circuit.



AC Plot of the Circuit

- We observe that the DC Gain of the circuit is around 30dB as expected.

- 
- Q2.asc
- Cursor 1
- V(v0)
- Freq: 46.131757MHz Mag: 11.619675m dB
- Phase: -299.11868°
- Group Delay: 1.6053036ns
- Cursor 2
- Freq: -N/A- Mag: -N/A-
- Phase: -N/A-
- Group Delay: -N/A-
- Ratio (Cursor 2 / Cursor 1)
- Freq: -N/A- Mag: -N/A-
- Phase: -N/A-
- Group Delay: -N/A-


```

P> E:\books\ST Devis\SEM 5\LLD\Assignment\Assignment 2\IG2.asc
--- Operating Point ---
V(vd): 2.04424 voltage
V(vg): 0.0 voltage
V(vd1): 0.199995 voltage
V(vd4): 1.8 voltage
V(vg01): 4.5e-16 voltage
V(v0): 2.04424e-08 voltage
V(v01): 0 voltage
I(dM1): 1e-07 device_current
I(dM2): 0.0 device_current
I(bM1): -2.04226e-12 device_current
I(dM3): -9.99977e-08 device_current
I(C1): 1.99996e-19 device_current
I(C2): -2.04424e-18 device_current
I(C4): 1.02212e-26 device_current
I(C5): 1.99996e-19 device_current
I(C7): 7.22121e-27 device_current
I(C11): 1e-07 device_current
I(dM3): 6e-07 device_current
I(dM4): 6e-07 device_current
I(dM5): -2.04226e-18 device_current
I(R1): 9.99977e-08 device_current
I(dM2): 6e-19 device_current
I(W1): 6e-19 device_current
I(W2): -7e-07 device_current


```

5

### 3 Question 3

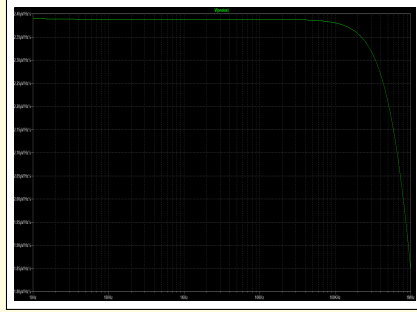

Noise Plot of the circuit

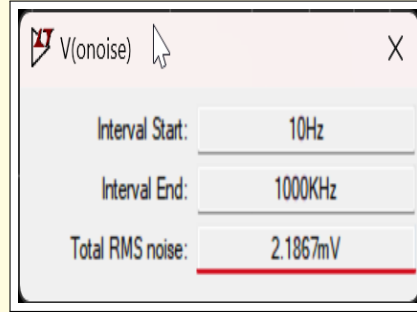

RMS value of the Noise

- Input Referred Noise =  $\frac{(1+\gamma g_m(r_0||R_L))kT}{g_m^2(r_0||R_L)^2 C_L}$
- The input noise is a white spectrum and the output noise is a combination of low frequency flicker noise and noise due to capacitive load.
- The Noise due to bias resistors is very very low.
- When we integrate the output noise over a 1MHz bandwidth, LTSpice gives us a value of 0.0021867. This is in V.
- Therefore, the noise power is  $6.06mV^2$
- From the analytical expression, we get total output noise as  $1.102mV^2$ , which is slightly less than the simulated value as we have not considered the non-idealities of the process and body effect.