

# Assignment 2

October 16, 2023

Total = 15 mark

Note:

- (1) Please follow the instructions given.
- (2) Plagiarism is strictly not allowed. If violated, zero marks will be awarded to all the stakeholders.

Design and simulate a 2-stage opamp using LT-Spice software in 180 nm technology. Highlight the frequency compensation technique used. The specifications are the following -

- 1) DC gain  $\geq 55$  dB
- 2) Unity gain frequency, UGF  $\geq 100$  MHz
- 3) Phase margin  $\geq 55$  degree
- 4) Supply voltage, VDD = 1.8 V
- 5) Power Budget  $\leq 300 \mu\text{W}$
- 6) The output swing should be as high as possible.

Please use the technology model file for 180 nm from the attachment given in the assignment with the name "PTM-PMOS-NMOS"

Include the following in the submission :-

- 1) Schematic of the design with all aspect ratios tabulated. 2 mark
- 2) Operating points of all devices and components. 2 mark
- 3) Magnitude and phase response plots highlighting DC gain, UGF, and phase margin. 2+2+2 = 6 mark
- 4) Report input common-mode range (ICMR) and output common-mode range (OCMR). 1+1 = 2 mark
- 5) Connect the designed opamp in unity feedback configuration and apply 100 mV peak-to-peak sine wave with frequency of 1KHz and frequency of 100 MHz. Plot input and output waveforms for both the cases. What do you infer from the results? Justify it. 2+1 = 3 mark