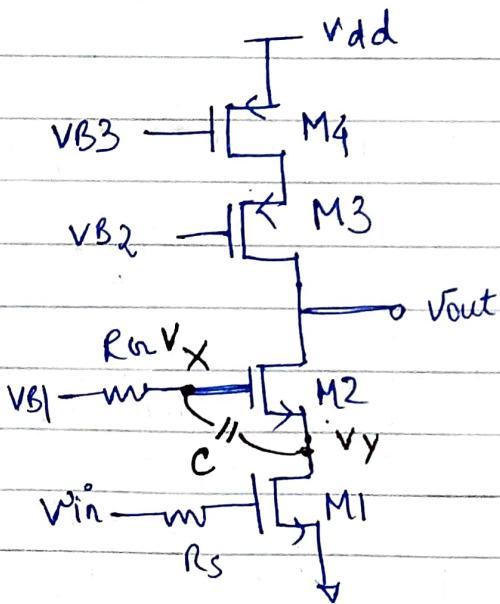


Tutorial-6 Solutions

81) After laying out the given typical single-stage cascode amplifier, a parasitic resistance $R_{Gn} = 1\text{ k}\Omega$ was observed at the gate of M2 as shown. Assume that C_{gs} of M2 is the only other parasitic significant enough to contribute, find the magnitude $|Av|$ of gain at 50Hz. (with at most 1% deviation from exact answer). Assume $R_s = 8\text{ k}\Omega$, $g_{m3} = g_{m4} = 1\text{ mS}$, $g_{m1} = g_{m2} = 8\text{ mS}$, g_{ds} of all transistors as $48A/\text{V}\text{S}$, $C_{gs2} = 76\text{ pF}$.




$$g_{mp} = g_{m3} = g_{m4} = 1\text{ mS}$$

$$g_{mn} = g_{m1} = g_{m2} = 8\text{ mS}$$

Solution

Small signal picture :

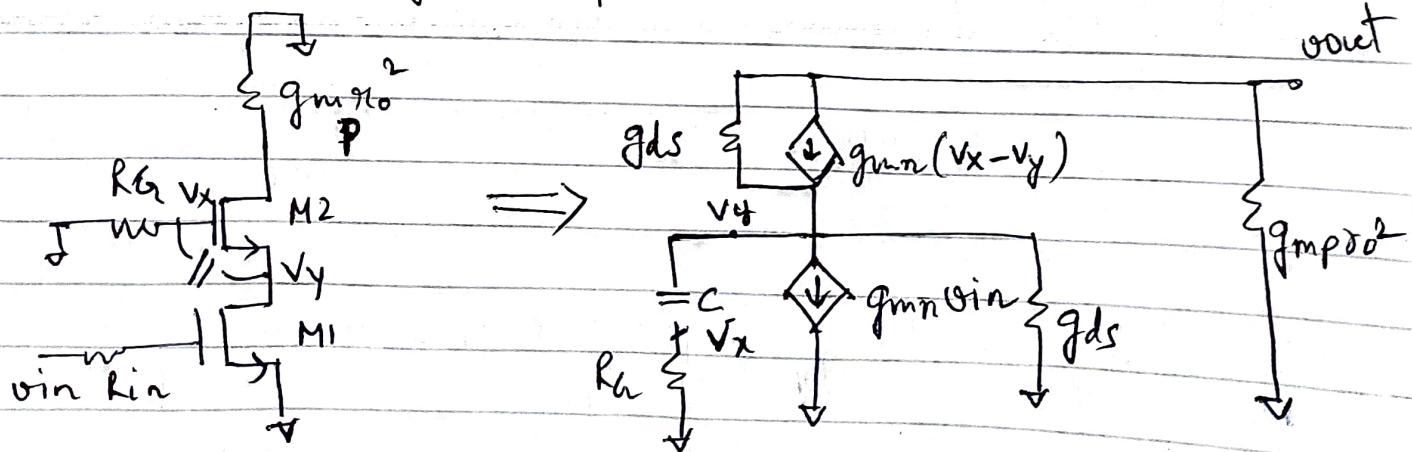

KCL at node out,

$$\frac{v_{out}}{gmp^{20^2}} + gds(v_{out} - v_y) + gmn(v_x - v_y) = 0 \quad (1)$$

And, $\frac{v_x}{R_a} = (v_y - v_x) sc$

$$\Rightarrow v_y = \left(\frac{1}{R_a sc} + 1 \right) v_x \quad (2)$$

Wing (2) in (1),

$$v_{out} \left[\frac{1}{gmp^{20^2}} + gds \right] - gds \left(\frac{1}{R_a sc} + 1 \right) \frac{v_x}{R_a sc} - \frac{gmn v_x}{R_a sc} = 0$$

$$\Rightarrow \frac{v_{out}}{v_x} = \frac{\left[\frac{gmn + gds}{R_a sc} + gds \right]}{\left[\frac{1}{gmp^{20^2}} + gds \right]} \approx \frac{\frac{gmn}{R_a sc} + gds}{\frac{1}{gmp^{20^2}} + gds} \quad (3)$$

KCL at node Y,

$$\frac{v_y}{R_a + \frac{1}{sc}} + gmn v_{in} + gds v_y = \frac{0 - v_{out}}{gmp^{20^2}}$$

$$\Rightarrow v_y \left[gds + \frac{1}{R_a + \frac{1}{sc}} \right] + gmn v_{in} = \frac{-v_{out}}{gmp^{20^2}} \quad (4)$$

Using (2) in (4),

$$v_x \left(1 + \frac{1}{R_{asc}} \right) \left(g_{ds} + \frac{sc}{1+R_{asc}} \right) + g_{mn} v_{in} = \frac{-v_{out}}{gm_p s_0^2}$$

$$\Rightarrow v_x \left[\frac{R_{asc} + 1}{R_{asc}} \right] \left[\frac{g_{ds}(1+R_{asc}) + sc}{1+R_{asc}} \right] + g_{mn} v_{in} = \frac{-v_{out}}{gm_p s_0^2}$$

$$\Rightarrow v_x \left[\frac{g_{ds}[1+R_{asc}] + sc}{R_{asc}} \right] + g_{mn} v_{in} = \frac{-v_{out}}{gm_p s_0^2}$$

— (5)


Using (3) in (5),

$$\Rightarrow g_{mn} v_{in} + \frac{v_{out}}{R_{asc}} \left[\frac{g_{ds}(1+R_{asc}) + sc}{\frac{g_{mn}}{R_{asc}} + g_{ds}} \right] \left[\frac{1}{gm_p s_0^2} + g_{ds} \right] = \frac{-v_{out}}{gm_p s_0^2}$$

$$g_{mn} v_{in} = -v_{out} \left[\frac{g_{ds}(1+R_{LSC}) + SC}{g_{mn} + g_{ds}(R_{LSC})} \left(\frac{1}{g_{mp} s_{10}^2} + g_{ds} \right) + \frac{1}{g_{mp} s_{20}^2} \right]$$

$$\Rightarrow \frac{v_{out}}{v_{in}} = -\frac{g_{mn}}{\left[\frac{g_{ds}(1+R_{LSC}) + SC}{g_{mn} + g_{ds} R_{LSC}} \left(\frac{1}{g_{mp} s_{20}^2} + g_{ds} \right) + \frac{1}{g_{mp} s_{20}^2} \right]_{(ans)}}}$$

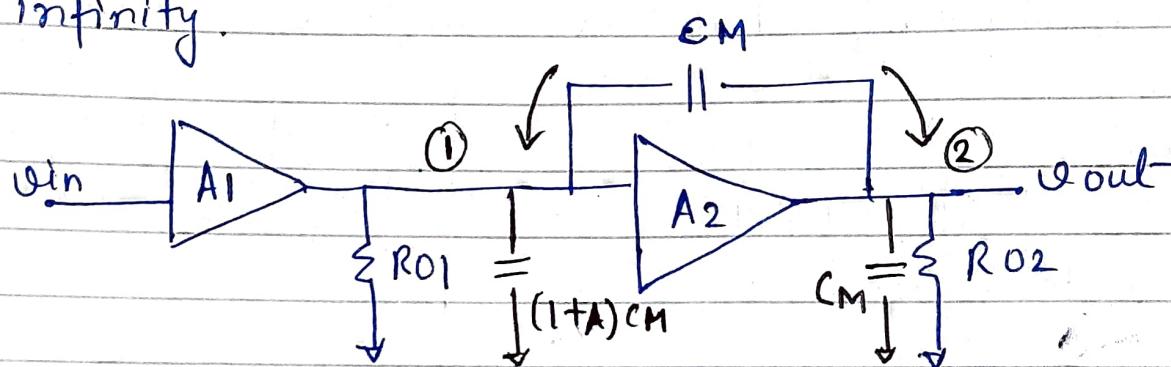Q2) Find the 3dB bandwidth of the circuit shown below in Hz. Given A_1 is a non inverting amplifier with a gain of 464 and output impedance $R_{O1} = 13\text{M}\Omega$. A_2 is an inverting amplifier with a gain of 16, output impedance $R_{O2} = 20\text{M}\Omega$, $C_M = 5\text{pF}$ and assume input impedance of both amplifiers as infinity.



Solution:

$$\begin{aligned} \text{Pole frequency at } ① &\Rightarrow \frac{1}{2\pi R_{O1} (1+A) C_M} \\ &= \frac{1}{2\pi (13\text{M}\Omega) (1+464) (5\text{pF})} \\ &= 144.104 \text{ Hz.} \end{aligned}$$

$$\begin{aligned} \text{Pole frequency at } ② &\Rightarrow \frac{1}{2\pi R_{O2} C_M} \\ &= \frac{1}{2\pi (20\text{M}\Omega) (5\text{pF})} = 1.592 \text{ kHz.} \end{aligned}$$

$$\begin{aligned} \therefore 3\text{dB bandwidth / freq.} &= \text{dominant pole frequency} \\ &= 144.104 \text{ Hz.} \end{aligned}$$


(Ans)

(Q3) In the circuit shown below, A₁, A₂ and A₃ are 3 ideal voltage amplifiers having DC gain of K, -K and K respectively. Then the total phase shift obtained (in degrees) in the loop at a frequency of 2.2 MHz when they are connected in unity feedback is given by $\pm 180^\circ - X^\circ$. Find the value of X.

Given : $R = 2.2 \text{ k}\Omega$
 $C = 19 \text{ pF}$


(Ans. upto 3 decimal places)

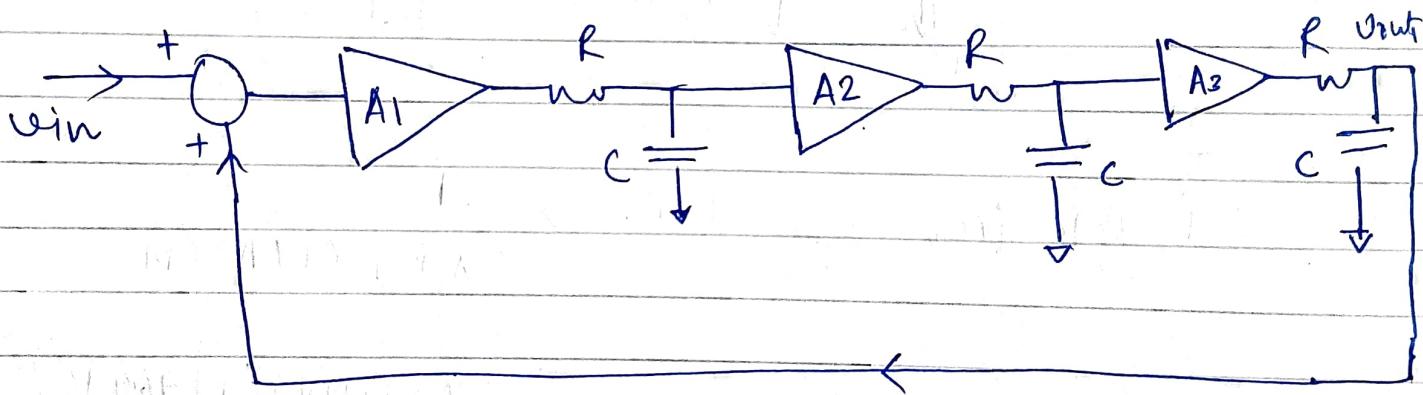Ideal volt ampl.
 $R_{in} \rightarrow \infty$
 $R_{out} \rightarrow 0$



Solution : Find total phase shift in loop :-

Find loop transfer function,

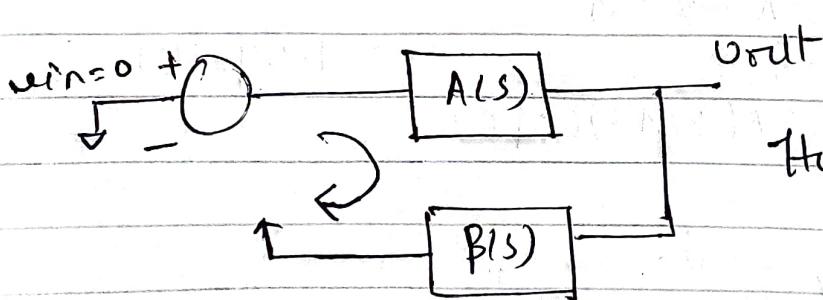

Here, loop transfr function = $A(s) f(s)$.

For given circuit,
 $B(s) = 1$

$$A(s) = \frac{A_1 A_2 A_3}{(1 + R_s s)^3}$$

$$A(s) \beta(s) = \frac{-k^3}{(1 + R_s s)^3}$$

Total phase shift $\Rightarrow \pm 180^\circ - \tan^{-1}$

Putting $s = j\omega$,

$$A(j\omega) \beta(j\omega) = \frac{-k^3}{(1 + j\omega R_C)(1 + j\omega R_C)(1 + j\omega R_C)}$$

$$\therefore \text{Phase Shift in loop} = \pm 180^\circ - \tan^{-1}(wR_C) - \tan^{-1}(wR_C) - \tan^{-1}(wR_C)$$

$$= \pm 180^\circ - \underbrace{3 \tan^{-1}(wR_C)}_{X^\circ}$$

$$X^\circ = 3 \tan^{-1} \left(2\pi (2.2 \text{ MHz}) (2.2 \text{ k}\Omega) (19 \text{ pF}) \right)$$

$$\Rightarrow X^\circ = 3 \tan^{-1}(0.5775)$$


$$\Rightarrow X^\circ = 90.02^\circ \quad (\text{Ans})$$

q4) Given below is an amplifier A, containing 2 stages.

A_1 and A_2 , with an open loop DC gain of 60 dB. The first dominant pole f_{p1} is at node X and is equal to 6 MHz. The second dominant pole frequency f_{p2} is at node Y and is equal to 25.4 MHz. If this amplifier is needed to be operated in closed loop, some frequency


compensation must be done in A₁ to ensure its stability. To do so, the first dominant pole is lowered to a frequency f_{P1}' by adding a capacitor C_M between nodes X and Y.

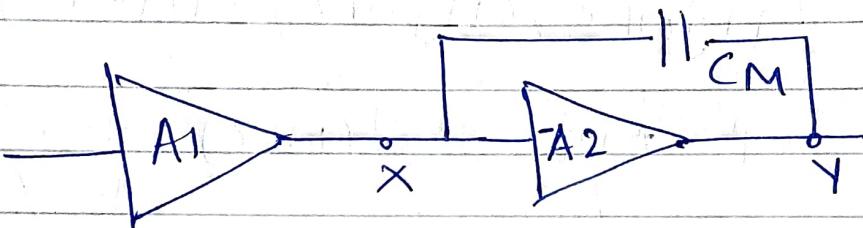Determine the factor by which capacitance at node X increases after performing frequency compensation. Assume second dominant pole's location remains unchanged.



Solution: Amplifier A₁'s open loop dc gain is 60dB (overall).

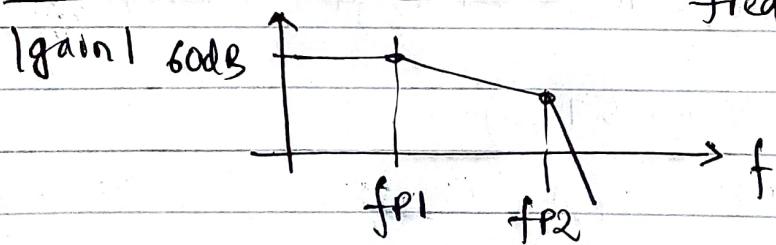
Before compensation suppose: (Open loop amp's freq. response)



To ensure stability of A in closed loop means effectively it is desired to make A a first order system (single pole only before unity gain frequency). ~~and then~~ using compensation and then use it in closed loop.

Limiting case: Make gain at $f_{P2} \rightarrow 0\text{dB}$ to make A a first order system.

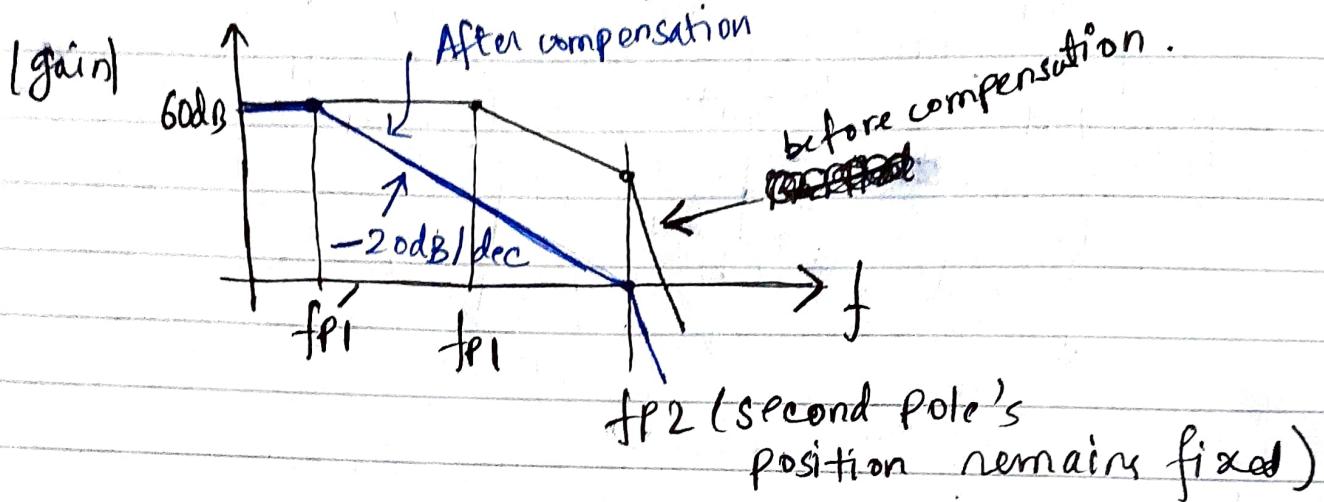After compensation : (still open loop amp's frequency response) .



∴ From f_{p1}' to f_{p2} , there is a 60 dB fall in magnitude.

$$\therefore f_{p1}' = \frac{f_{p2}}{10^3} \quad [\text{per decade, } -20 \text{ dB}]$$

Since $f_{p1}' < f_{p1}$, $Cx' > Cx$ and $f = \frac{1}{2\pi R C}$,

$$\frac{Cx'}{Cx} = \frac{f_{p1}}{f_{p1}'}$$


$$\Rightarrow \frac{Cx'}{Cx} = \frac{f_{p1}}{f_{p2}} \times 1000$$

$$\Rightarrow \frac{Cx'}{Cx} = \frac{6 \text{ MHz}}{25.4 \text{ MHz}} \times 1000 = 236.22$$

(Ans)

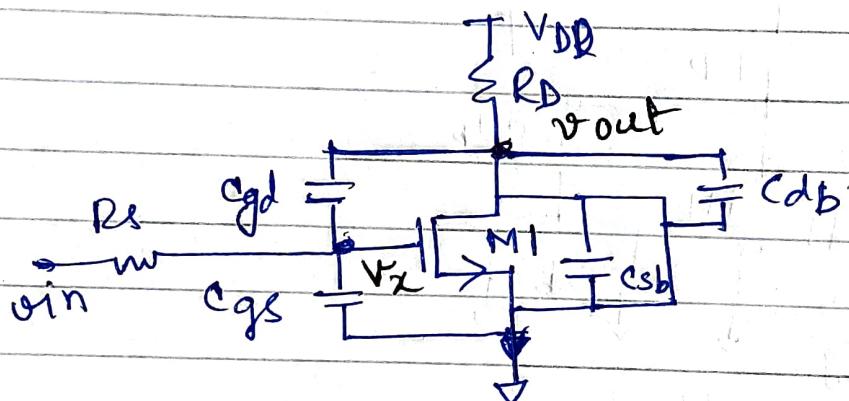Q5) A simple common source amplifier, like the one shown below, starts behaving like a multi-pole system at high frequencies. Try to locate the dominant pole (closest to origin) in M rad/sec.

$$C_{GS} = 6 \text{ fF}, C_{DB} = 17 \text{ fF}, C_{SB} = 6 \text{ fF}, C_{GD} = 17 \text{ fF}, g_m = 19 \text{ mS}, R_S = 18 \text{ k}\Omega, R_D = 18 \text{ k}\Omega.$$



Solution : 2 methods for solving this,

a) Direct approach

$$\frac{(v_x - v_{in})}{R_s} + \omega_x s C_{GS} + (v_x - v_{out}) s C_{GD} = 0 \quad (1)$$

$$\text{and, } (v_{out} - v_x) s C_{GD} + g_m \omega_x + v_{out} \left(\frac{1}{R_D} + s C_{DB} \right) = 0$$

$$\Rightarrow \omega_x = \frac{v_{out} (s C_{GD} + \frac{1}{R_D} + s C_{DB})}{g_m - s C_{GD}} \quad (2)$$

Substituting (2) in (1),

$$\frac{v_{out}}{v_{in}} = \frac{-(g_m - sC_{gd})R_D}{s^2(R_s R_D C') + s(g_m R_D R_s C_{gd} + R_s C_{gs} + R_D(C_{gd} + C_{db})) + 1}$$

where, $C' = C_{gs} C_{gd} + C_{db} C_{gs} + C_{gd} C_{db}$

Roots of denominator \rightarrow gives you pole frequencies.

b) Second method (Approximate but quick approach).

Equivalent capacitance at node X = $C_{gs} + (1 + |Av|)C_{gd}$

$$\Rightarrow C_X = C_{gs} + (1 + g_m R_D)C_{gd}$$

Equivalent resistance ~~at node X~~ = $R_s \parallel \infty$
across C_X (R_X)
= R_s

$$\therefore \text{Pole at } X = \frac{1}{R_X C_X}$$

$$= \frac{1}{R_s [C_{gs} + g_m R_D C_{gd}]}$$

Similarly,

Eq. cap at V_{out} ,

$$C_{out} = C_{db} + C_{gd} \left(1 + \frac{1}{|Av|} \right)$$

$$= C_{db} + C_{gd} \left(1 + \frac{1}{g_m R_D} \right)$$

$$\approx C_{db} + C_{gd}$$

$$\therefore \text{pole at vout} = \frac{1}{R_D(C_{db} + C_{gd})}$$

$$\therefore \text{pole}(x) = 9.545 \text{ Mrad/sec}$$

$$\text{Pole}(out) = 1.633 \times 10^6 \text{ Mrad/sec}$$


Pole(x) \rightarrow closest to origin \rightarrow dominant pole
(ans)

Q6) Calculate the aspect ratio ($\frac{W}{L}$) of M5.

Given $V_{S4H} = V_{S4L}$, $L_6 = L_4$, $W_6/W_4 = 23.2$,

$$W_7/L_7 = 2, |V_{TP3}| = |V_{TP4}| = |V_{TP6}|,$$

$$V_{TN8} = V_{TN5} = V_{TN7}.$$

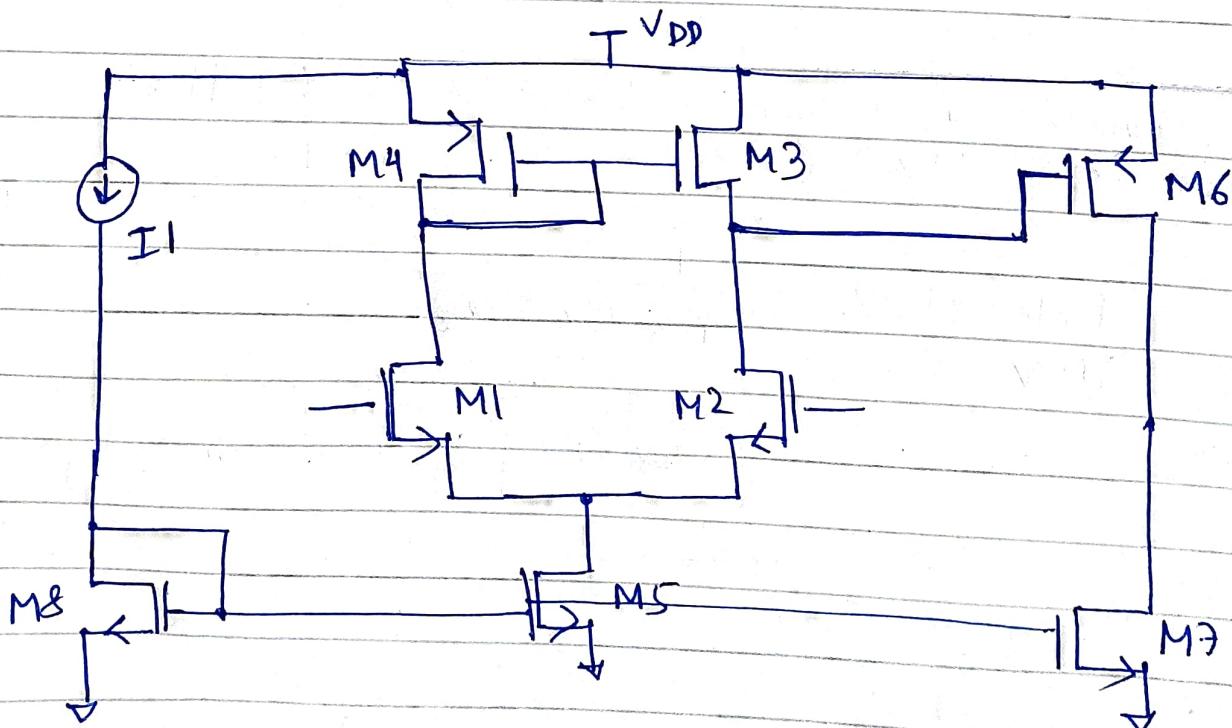

Solution:

$$V_{SD4} = V_{SD6}$$

$$\Rightarrow |V_{TP4}| + V_{SD, \text{sat}4} = |V_{TP6}| + V_{SD, \text{sat}6}$$

$$\Rightarrow V_{SD, \text{sat}4} = V_{SD, \text{sat}6}$$

$$\Rightarrow \sqrt{\frac{2I_4}{\mu_{p\text{cox}}\left(\frac{W}{L}\right)_4}} = \sqrt{\frac{2I_6}{\mu_{p\text{cox}}\left(\frac{W}{L}\right)_6}}$$

$$\Rightarrow \frac{(W/L)_6}{(W/L)_4} = \frac{I_6}{I_4} = \frac{I_7}{I_{5/2}} = \frac{2I_7}{I_5} - (1)$$

and, ~~$V_{AS5} = V_{AS7}$~~

$$\frac{(W/L)_7}{(W/L)_5} = \frac{I_7}{I_5} = \frac{1}{2} \left[\frac{(W/L)_6}{(W/L)_4} \right]$$

↑ from (1).

$$\therefore (W/L)_5 = 2 \frac{(W/L)_7}{(W/L)_6} (W/L)_4$$


$$\Rightarrow \left(\frac{W}{L}\right)_5 = \frac{2 \times 2}{23 \cdot 2} = 0.172 \quad (\underline{\underline{Ans}})$$

Q1) Calculate the magnitude $|A_{CM}| = \left| \frac{V_{O1} - V_{O2}}{V_{CM, \text{in}}} \right|$ if

there is a mismatch in the transconductance of M1 and M2. Assume $gm_1 = gm + \frac{\delta gm}{2}$ and

$g_{m2} = g_m - \frac{\delta g_m}{2}$, where $\frac{\delta g_m}{g_m} = 0.01$. Take
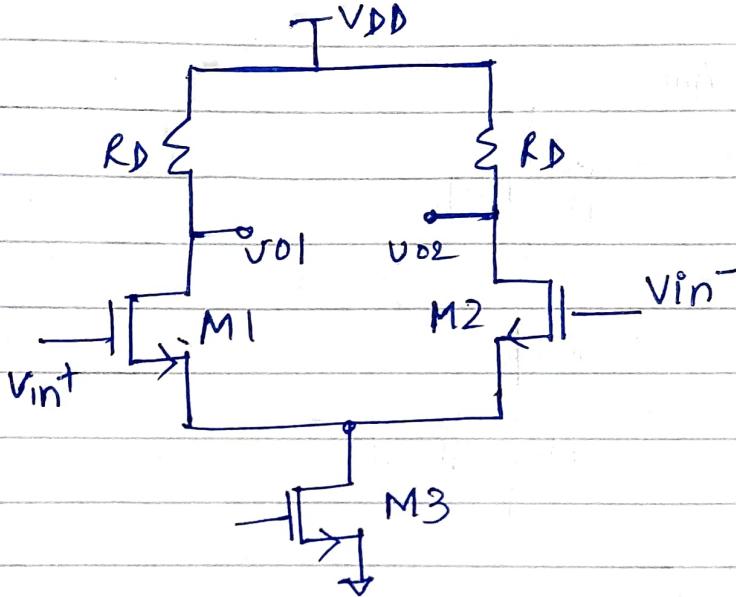
$$g_m = 200 \mu A/V, n_{O3} = 85 k\Omega, R_D = 58 k\Omega.$$



Solution:

$$|A_{CM}| = \left| \frac{v_{o1} - v_{o2}}{v_{cm}} \right|$$

$$v_{o1} - v_{o2} = \frac{-(g_m + \frac{\Delta g_m}{2}) R_D v_{cm}}{1 + g_m (2 R_S)} + \frac{(g_m - \frac{\Delta g_m}{2}) R_D v_{cm}}{1 + g_m (2 R_S)}$$


$$\Rightarrow |A_{CM}| = \left| \frac{v_{o1} - v_{o2}}{v_{cm}} \right| = \left| \frac{-\Delta g_m R_D}{1 + g_m (2 R_S)} \right|$$

$$\Delta g_m = (0.01)(g_m) = (0.01)(200 \mu A/V)$$


$$\Rightarrow |A_{CM}| = \frac{(2 \times 10^{-6})(58 \times 10^3)}{1 + (200 \times 10^{-6})(2 \times 85 \times 10^3)} = 0.003314$$

(Ans)

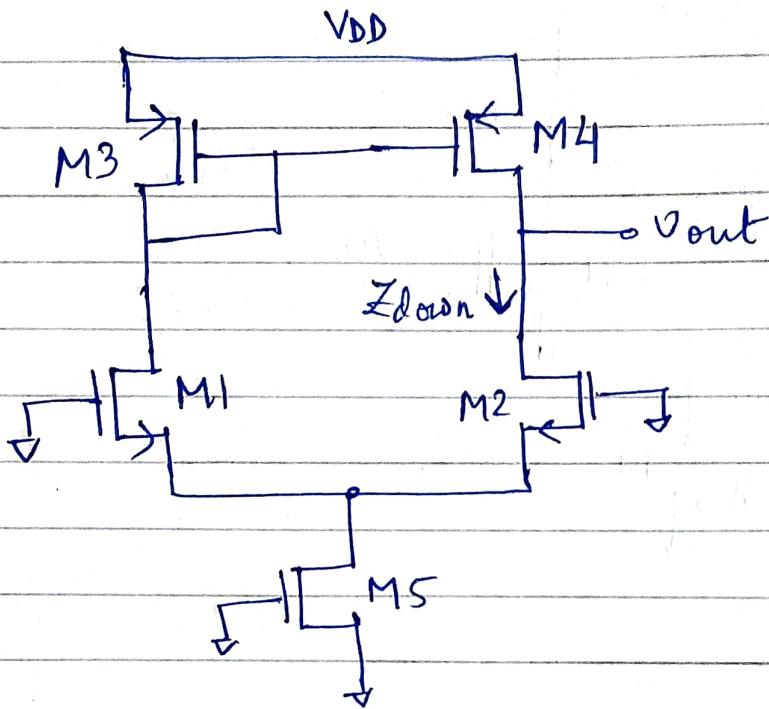(Q8) In the below figure, calculate the downward impedance from 'V_{out}' node in M₂. Given $g_{m1} = g_{m2} = 735 \mu S$, $g_{m3} = 589.5 \mu S$, $I_5 = 32.6 \mu A$, $\lambda_1 = \lambda_2 = \lambda_3 = \lambda_4 = 10 mV^{-1}$.



Solution:

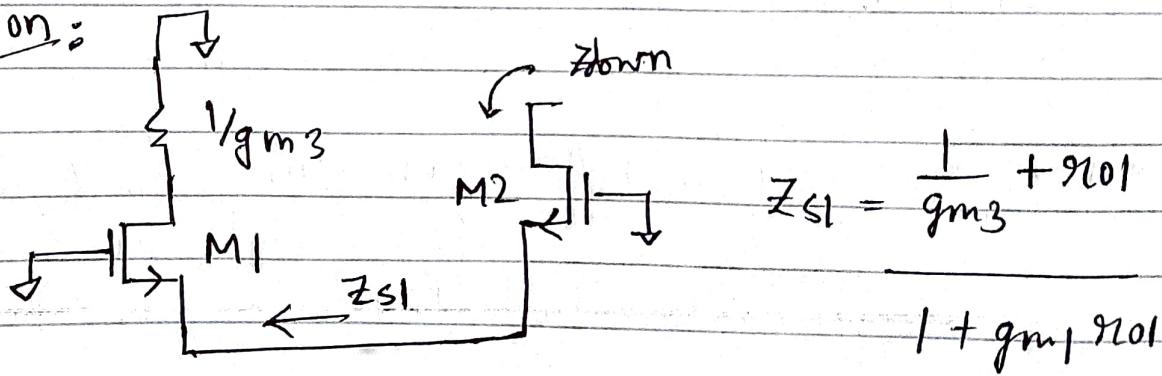

$$Z_{S1} \approx \frac{1}{g_{m1}}$$


$$Z_{down} = (1 + g_{m2} r_{o2}) Z_{S1} + r_{o2}$$

$$\Rightarrow Z_{down} = \frac{1}{g_{m1}} + \frac{g_{m2}}{g_{m1}} r_{o2} + r_{o2}$$

$$\begin{aligned}
 Z_{\text{down}} &= r_{01} + r_{02} \quad (\text{as } g_{m1} = g_{m2}) \\
 &= 2r_{02} \quad (r_{01} = r_{02}) \\
 &= \frac{2}{\lambda_2 \times \left(\frac{I_5}{2}\right)} = \frac{2}{(10 \mu V^{-1}) \left(\frac{32.64 A}{2}\right)}
 \end{aligned}$$

$$Z_{\text{down}} = 12.26 \text{ M}\Omega \quad (\text{Ans})$$

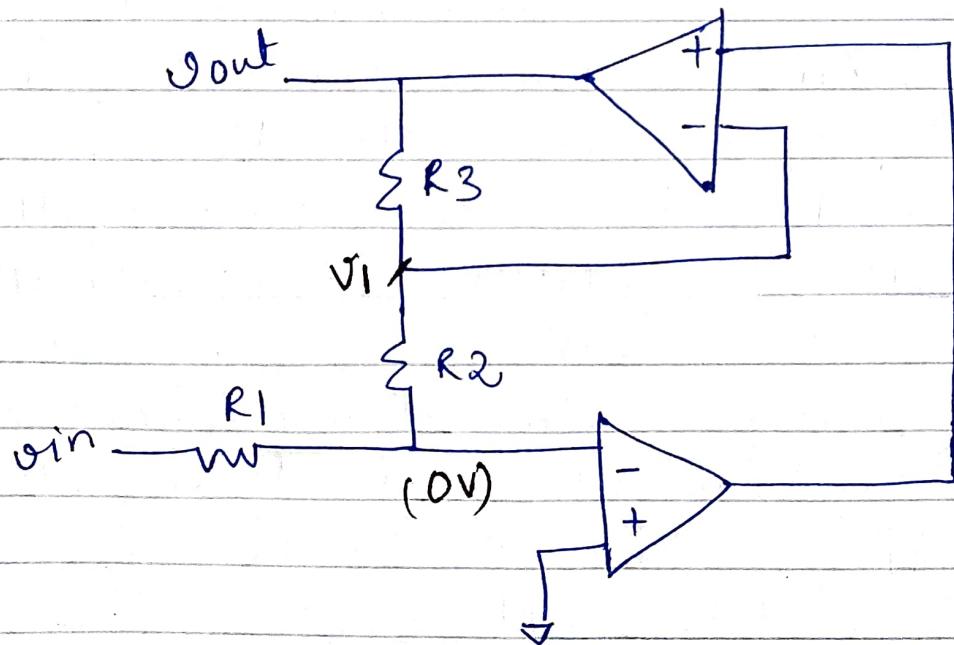
Q9) In the circuit shown below, opamp is ideal. Find V_{out} . Given $R_1 = 3k\Omega$, $R_2 = 1k\Omega$, $R_3 = 9k\Omega$, $V_{\text{in}} = 3V$. (Accuracy = ± 0.001)




Solution :

Ideal opamp $\Rightarrow A \rightarrow \infty, R_{\text{in}} \rightarrow \infty, R_{\text{out}} \rightarrow 0$.

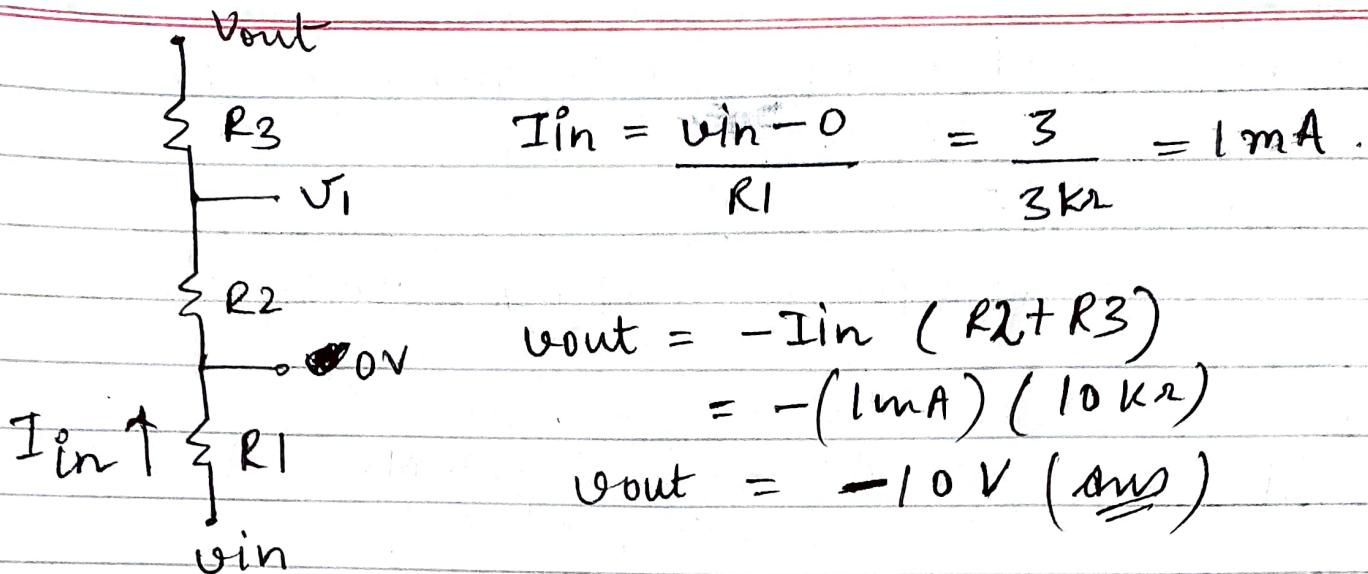
In the given circuit, virtual short is applicable.



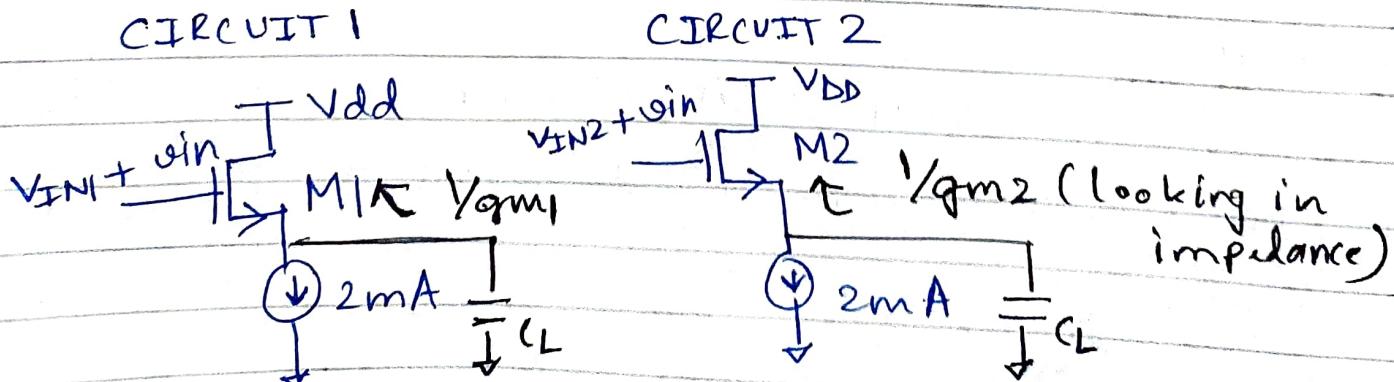Q10) In the circuit shown below, current source is ideal and the transistor is in saturation. Circuit 1 and circuit 2 have different DC levels V_{IN1} , V_{IN2} with small signal v_{in} and same output common mode at source node. Circuit 1 and circuit 2 have a 3dB bandwidth (BW) of $100M\text{rad/sec}$, $187M\text{rad/sec}$ respectively. while driving the same load of 6 pF . New circuit is made by connecting circuit 1 and circuit 2. Find the 3dB BW (in $M\text{rad/sec}$) of new CIRCUIT which is driving same load 6 pF .



NEW CIRCUIT

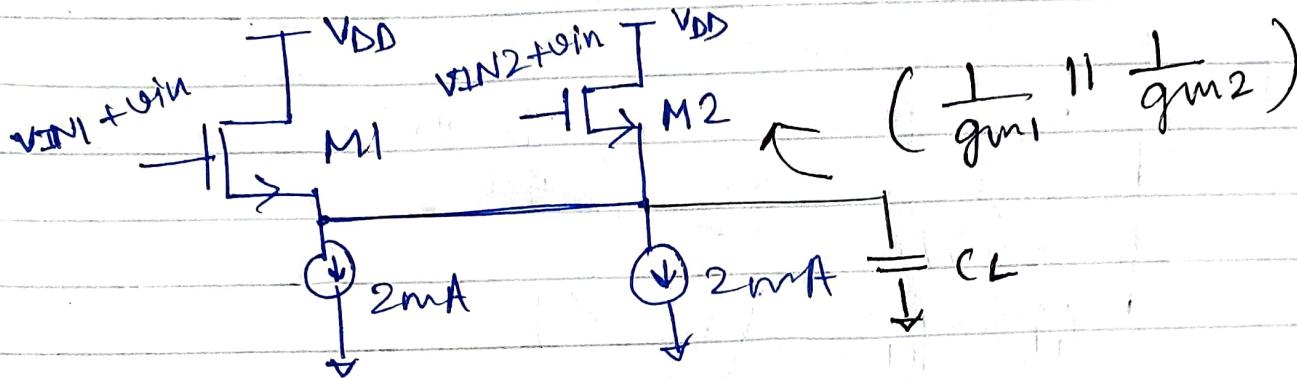

Solution :

$$3\text{dB BW of circuit 1} = \omega_1 = \frac{gm_1}{C_L}$$

$$\Rightarrow gm_1 = \omega_1 C_L \\ = (100\text{M})(6\text{p})$$

$$\Rightarrow gm_1 = 600\text{4S}$$

$$3\text{dB BW of circuit 2} = \omega_2 = \frac{gm_2}{C_L}$$

$$\Rightarrow gm_2 = \omega_2 C_L \\ = (187\text{M})(6\text{p})$$

$$\Rightarrow gm_2 = 1122\text{4S}$$

$$\therefore 3\text{dB BW of new circuit} = \frac{gm_1 + gm_2}{C_L}$$

$$\Rightarrow \omega = \frac{\omega_1 C_L + \omega_2 C_L}{C_L} = \omega_1 + \omega_2 \\ = 287\text{ Mrad/sec}$$

(Ans)