



भारतीय प्रौद्योगिकी संस्थान दिल्ली  
INDIAN INSTITUTE OF TECHNOLOGY DELHI

मुख्य परीक्षा उत्तर पुस्तिका  
MAJOR TEST ANSWER BOOK

नाम  
Name..... T PRATHAM .....

अनुक्रमांक  
Entry No. 2020EE30559

पाठ्यक्रम सं.  
Course No. ELL304 ग्रुप संख्या Group No. 01

पाठ्यक्रम शीर्षक  
Course Title Analog Integrated Circuits

दिनांक  
Date 19-11-2022

प्रयोग किए गए अनुवर्ती पृष्ठों की संख्या  
No. of continuation sheets used

प्रश्न सं. Q. No.	प्राप्त अंक Marks
1.	3.5
2.	1
3.	4.5
4.	5
5.	4
6.	
7.	
8.	
9.	
10.	
11.	
12.	
कुल TOTAL	18

पाठ्यक्रम निर्धारक के हस्ताक्षर और दिनांक  
Signature of Course Co-ordinator and date

अनुचित साधनों का प्रयोग करने वाले छात्रों को निलम्बित/निष्कासित किया जा सकता है।

Students using unfair means are liable to be punished by Suspension/Expulsion

परीक्षा केन्द्र में सेलफोन, काम्युनिकेटर्स व पीडीए साधनों का प्रयोग करना सख्त मना है।

Use of cell-phones, Communicators & PDAs in the Examination Hall is Strictly prohibited.

सभी पृष्ठों पर लिखें। Write on all pages.

Q5.


- a) Question: Which amplifier is used in most of the audio amplification systems? Design one such basic amplifier. What are its advantages and disadvantages over other type of amplifiers?

(3)

Answer:


A "class-D amplifier" or a "switching amplifier" is used in most of audio amplification systems today. It finds its application from in mobile phone speakers, hearing aids, home theater systems, subwoofers, bass amplifiers, RF amplifiers etc.

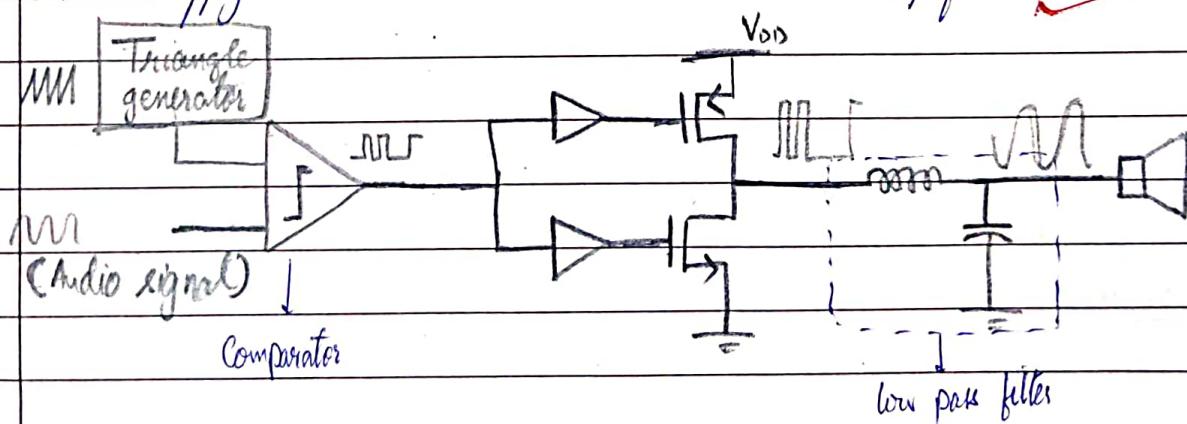In a class-D amplifier, the amplification device (MOSFET) acts as a switching device instead of a linear gain device as we have seen till now. It is fed a pulse width modulated (PWM) signal and its output rapidly switches between the supply rails. A basic class-D amplifier is shown below:



An audio signal is fed into a comparator along with a high frequency triangular or sawtooth signal to generate a PWM signal, which is then fed into MOSFETs. We can see that at a particular instant, only one of the nMOS or pMOS is ON depending on the PWM signal. And the output is one of the supply rails. Hence we get an amplified digital signal which is then passed through a low pass filter.

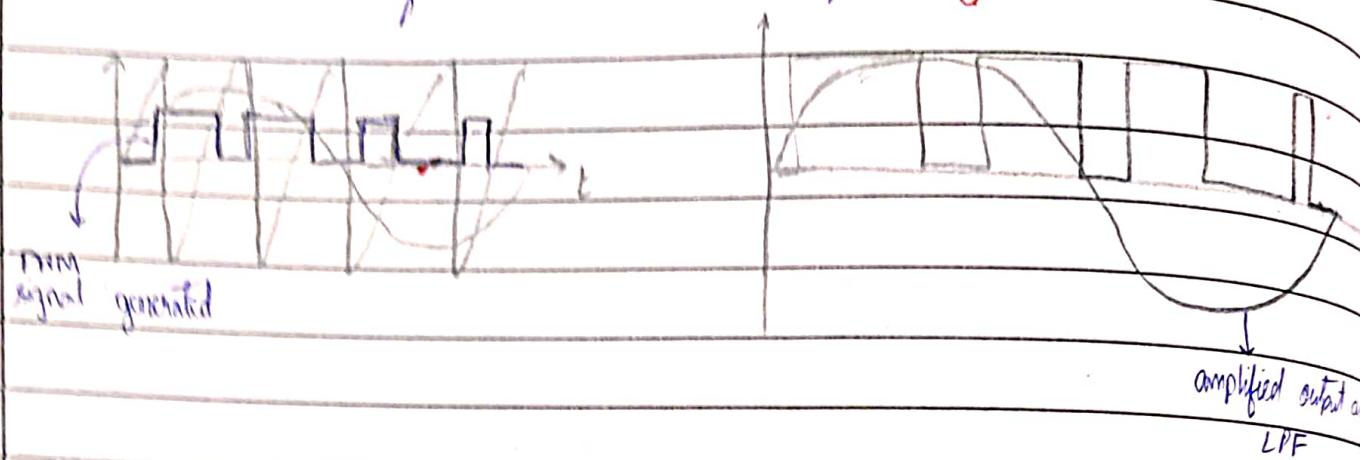through a low pass filter to remove the high frequency PMW carrier and we get an amplified audio signal which can be fed into a speaker.



The primary advantage of class-D amplifiers over class-A amplifiers (the ones which we have seen in class) is efficiency. Class-A amplifiers dissipate a lot of power and their efficiency is around 20-25% for most amplifiers. Whereas class-D amplifiers are as high as 90% efficient. This is particularly helpful where we want to transfer most of the power to the speaker, esp. in low power devices. But its primary disadvantage is a high THD.

More detailed analysis is beyond my time constraints here.


Justification: We have seen here a very helpful application of class-D amplifiers, and its particular usefulness in low power devices, as well as high power devices. Hence it is very flexible in its range of application.

- (1) b) As stated earlier, the amplifier described here is a class-D amplifier. The ideal characteristics of this amplifier is zero current ( $I_S$ ) when it is OFF ( $V_{GS} = 0$ ) and very low  $V_{DS}$  (ideally zero) when it is ON, and

instantaneous switching between ON and OFF regions ideally. That is it acts as an ideal switch.


Q1.

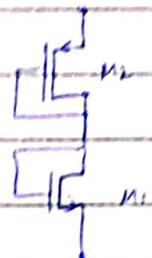- a) In figure 1a), both the MOSFETs are gate-drain connected, hence can be replaced by  $g_m$  and  $g_m'$  respectively.



$$\text{Hence total resistance} = \frac{1}{g_{m1}} + \frac{1}{g_{m2}}$$

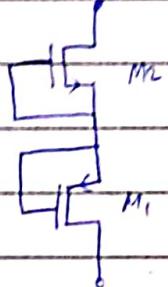In figure 1b) gate and source are shorted, which will only leave their drain-source resistances in series as the MOSFETs are OFF.



$$\text{Hence total resistance} = r_{ds1} + r_{ds2} \quad \text{X. 5}$$

So, the resistance in circuit b) is much larger than in a) b/w nodes X and Y.

- b) In this circuit, M2 is in ~~saturation~~ linear region since its gate width is ~~adjustable~~ ~~allow~~.


For M1, gate-drain are shorted :  $V_{ds} = V_{os}$  and  $V_{os} > V_{th}$

Now,  $V_{GS}$  of ~~M1~~ M2 is  $V_{GD2}$  of M2  $\rightarrow V_{GD2} > V_{th}$

$$\Rightarrow V_{th} - V_{D2} > V_{th}$$

$$\Rightarrow V_{GS2} - V_{th} > V_{D2} \rightarrow \text{linear region}$$

②

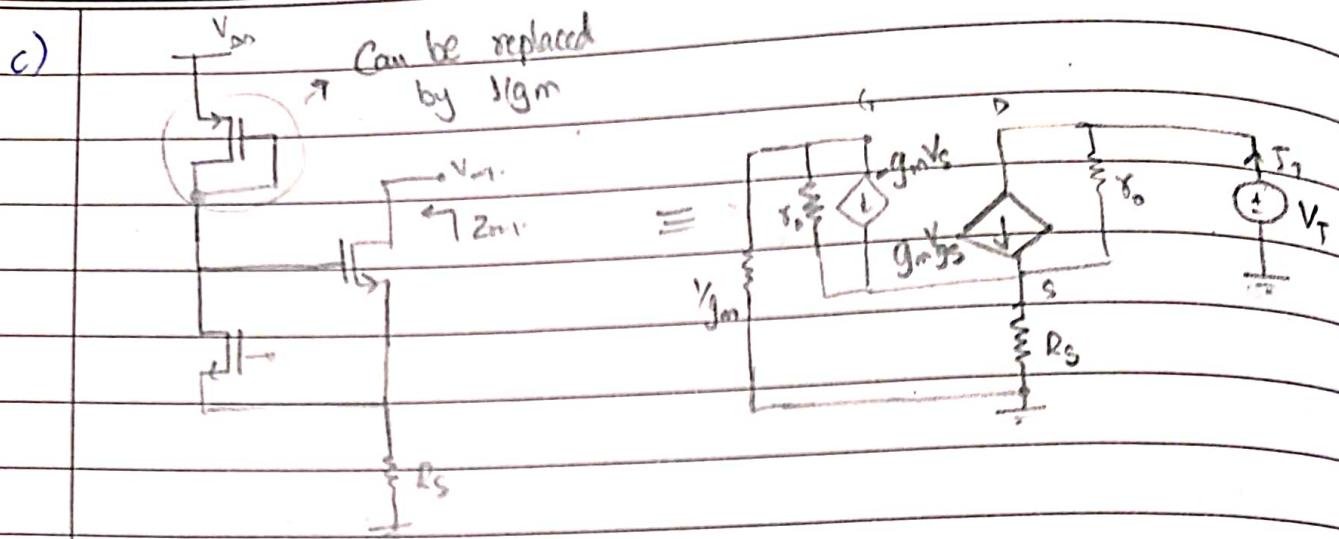

$$\text{KCL: } I_T = g_m V_{gs} + \frac{(V_T - V_s)}{r_o} \quad \text{--- (1)}$$

$$g_m V_g + \frac{(V_g - V_s)}{r_o} - g_m V_s = 0 \quad \text{--- (2)}$$

$$I_T + \frac{(V_g - V_s)}{r_o} - g_m V_s - \frac{V_s}{R_S} = 0 \quad \text{--- (3)}$$

From (2):  $V_g \left( \frac{1}{r_o} + g_m \right) = V_s \left( g_m + \frac{1}{r_o} \right)$

$$\Rightarrow V_g = V_s \quad \text{or} \quad V_{gs} = 0$$

$$(3): \quad I_T = \left( g_m + \frac{1}{R_S} \right) V_s$$

$$(4): \quad I_T = \frac{V_T}{r_o} - \frac{V_s}{r_o} \quad \text{--- (1)}$$

$$= \frac{V_T}{r_o} - \frac{I_T R_S}{(1 + g_m R_S) r_o}$$

$$\Rightarrow I_T \left( \frac{(1 + g_m R_S) r_o + R_S}{(1 + g_m R_S) r_o} \right) = \frac{V_T}{r_o} \quad \cancel{\times}$$

$$\therefore \frac{V_T}{I_T} = Z_{out} = \frac{g_m r_o R_S + r_o + R_S}{1 + g_m R_S}$$

$$\therefore \text{Output impedance} = \frac{g_m r_o R_S + r_o + R_S}{1 + g_m R_S}$$

62.

a)

### JCMR :-

$$V_{CM, min} = V_{DD} - V_{SD2,sat} - V_{SD1,sat} \approx V_{DD} - 3V_{ov} - V_{Th}$$

assuming  $V_{or}$  &  $V_{re}$  for  
all are equal.

$$V_{CM, \min} = V_{GS,7} + V_{TH}$$

$$= V_{ov} + 2V_{TH}$$

$$\therefore \text{JCMR} = V_{DD} - 4V_{ov} - 3V_{Th}$$


OCMR :-

$$\begin{aligned} V_{out,max} &= V_{DD} - V_{DS2,int} = V_{DS2,int} \rightarrow V_{G16} \quad | \quad V_{out,max} = V_{DD} - V_{DS2,int} \\ &= V_{DD} - 3V_{DD} = V_{IN} \quad \quad \quad = V_{DD} - V_{DD} \end{aligned}$$

$$V_{out,min} = V_{DS,off} + V_{GS,0}$$



$$OCMR = V_{DD} - 3V_{IN} - V_{IN}$$

## Frequency compensation :-

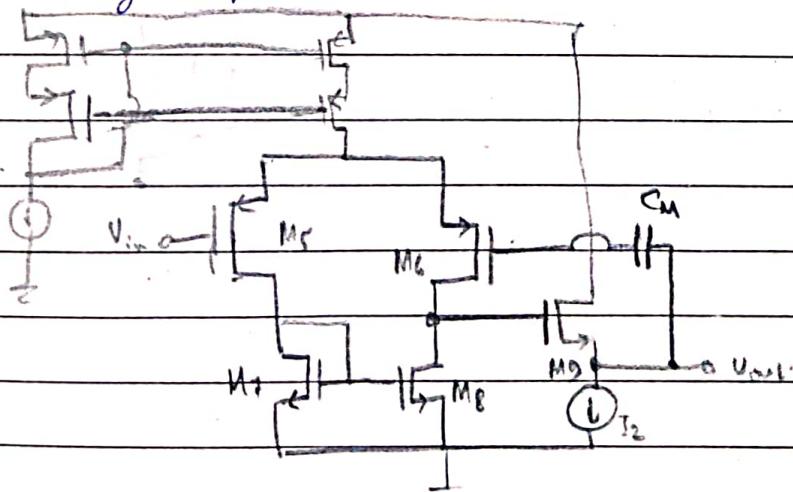

→ Miller b/w input &  
output of inverting amp.

b)

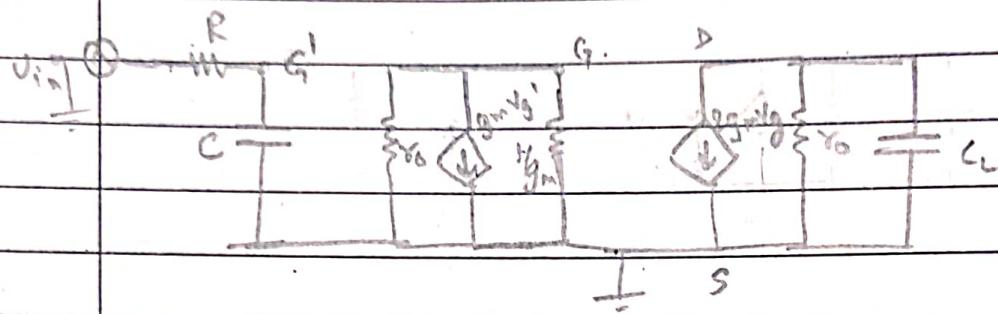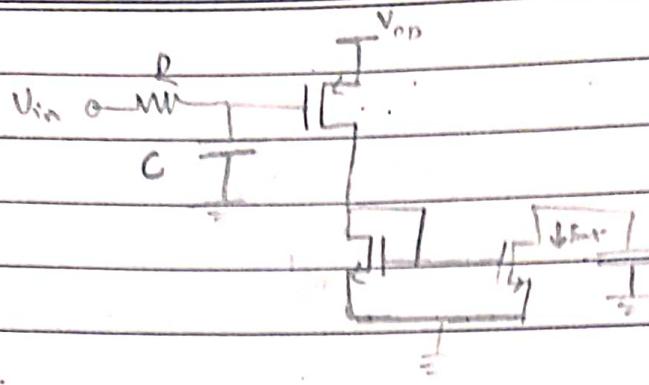

$$\text{Output, } \omega_0 = \frac{1}{\sqrt{R C_L}}$$

Q3.

a)

DC current in  $M_7 = I_o + I_s$  ✓ (assuming same aspect ratio of all) (x 0.5)





Small signal current in  $M_1 = -g_m V_{in}$  ✓ (x 0.5)

$$\therefore J_a = I_o + I_s - g_m V_{in}$$

Output current,  $J_b = -g_m V_{in}$  (x 0.5)


~~But~~ Drain of  $M_5$  is a better current sensing node because in this type of current mirror, drain of  $M_5$  is a virtual ground. Reason not correct

b)

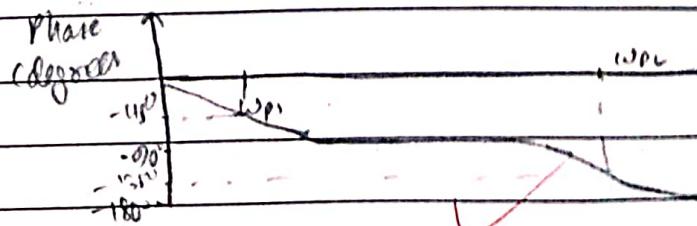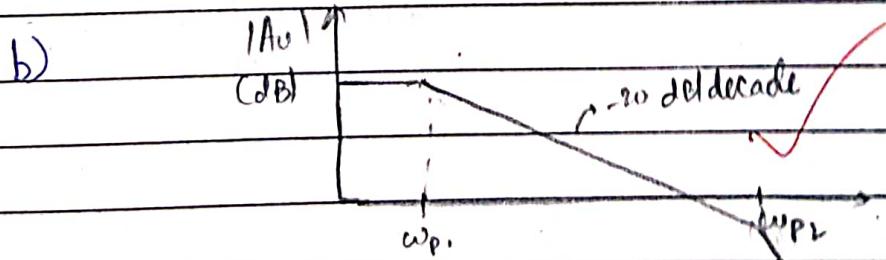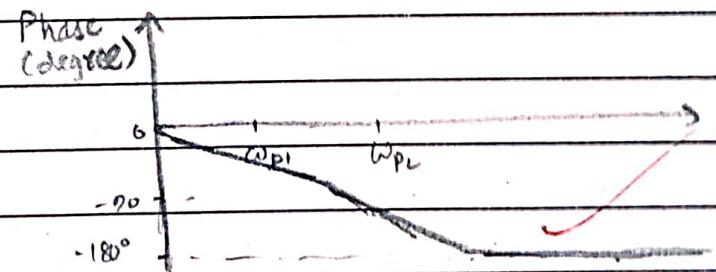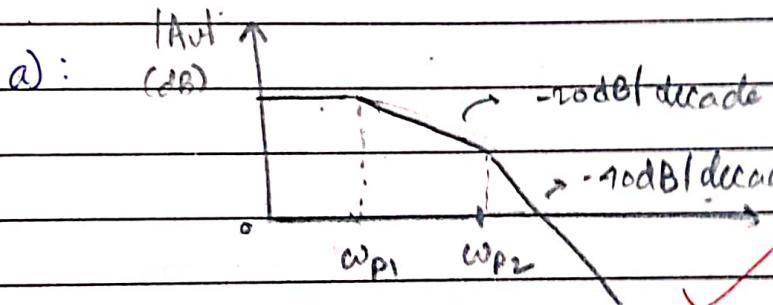

Configuration (a) might require frequency compensation

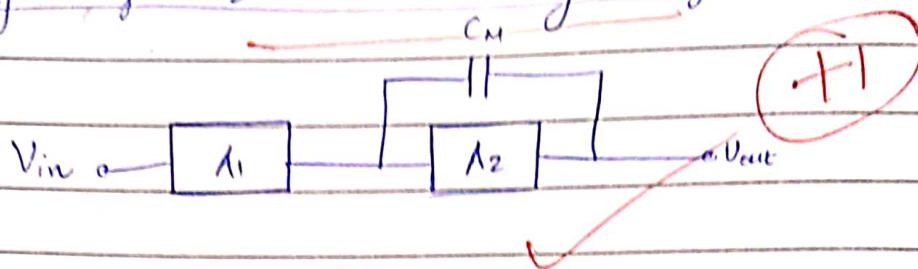Assuming stage  $A_2$  is inverting stage :-



Q4. a)

i) Half diff. ckt. :


Assuming  $\alpha$  equal for all  
& resistance of transistors  
in linear region  $R_T$ ,

we have a source degenerated circuit.

Hence small signal gain

$$= \frac{g_m R_D}{1 + g_m R_S}$$

$$= \frac{g_m (\beta_0 || R)}{1 + g_m (\beta_0 || R_T)}$$

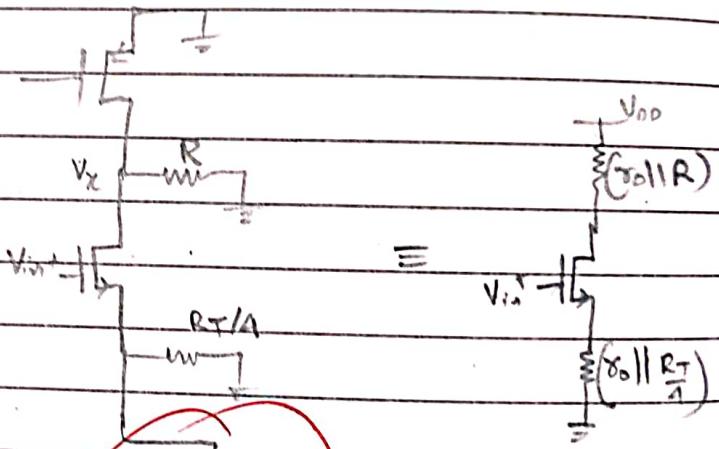

$\leftarrow$  does not appear in diff

2

ii) On node X:

$$\textcircled{1} \quad V_{X,\max} = V_{DD} - V_{SD,3} \\ = V_{DD} - V_{CV} - V_{Th}$$

} from above

$$V_{X,\min} = V_{DS,ext} = V_{AV}$$

} from below

$$\therefore OCMR = V_{AV} = 2 V_{AV} / V_{IN}$$

which is quite high indeed  
(assuming  $V_{AV}$  is same for all).

~~1~~ Symmetrically we can see on  $\gamma$  as well.

Hence, I agree that output swing available is quite high.

Reason is wrong

iii)  $M_7$  : Current source & biases  $M_6$

$M_8$  : load

(X)

$M_9$  : load

$M_{10}$  : Current mirror ~~load~~

$M_{11}$  : Current source and matches load for  $M_{10}$

Sets  $V_{O,cm} = V_{REF}$  using -ve feedback

iv) If output common mode variation is zero, then  $V_G$  of  $M_9$  is also zero.


Since in common mode,  $V_x$  &  $V_y$  have same potential.


Hence current in each  $R$  is zero.

Hence,  $V$  at between of  $R$  is ~~also~~ same as  $V_x$  which is zero.

2

12

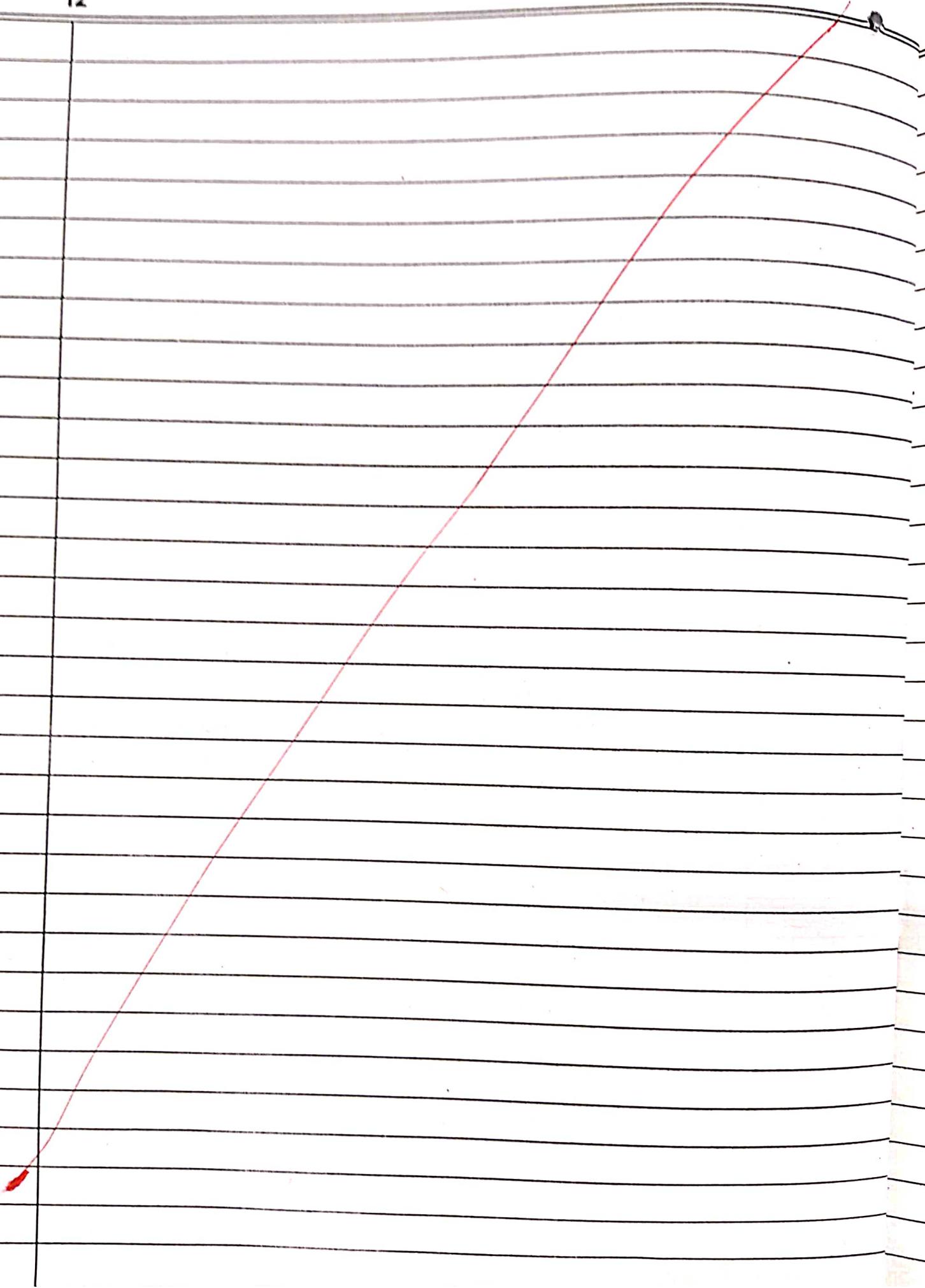

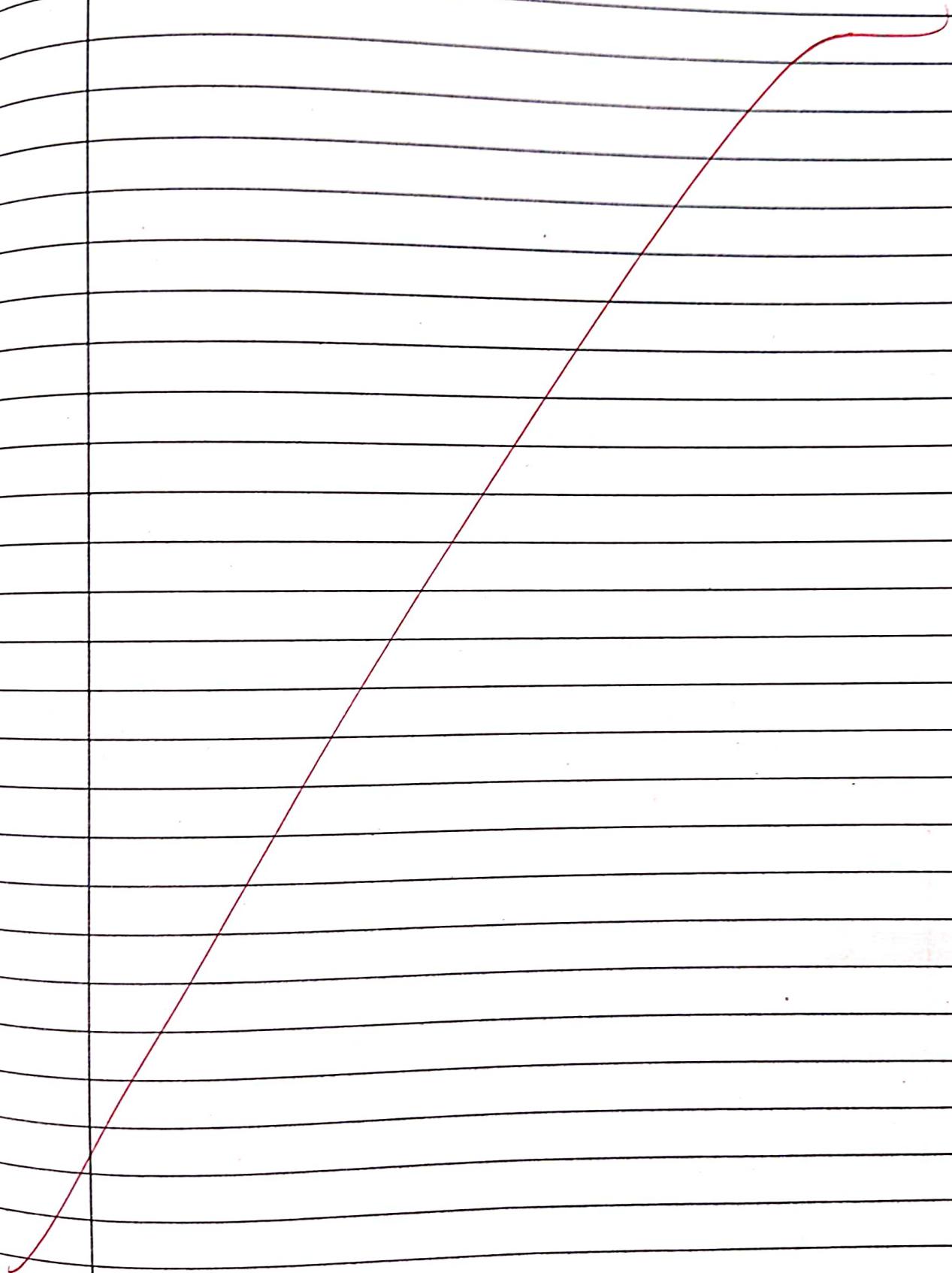

14

